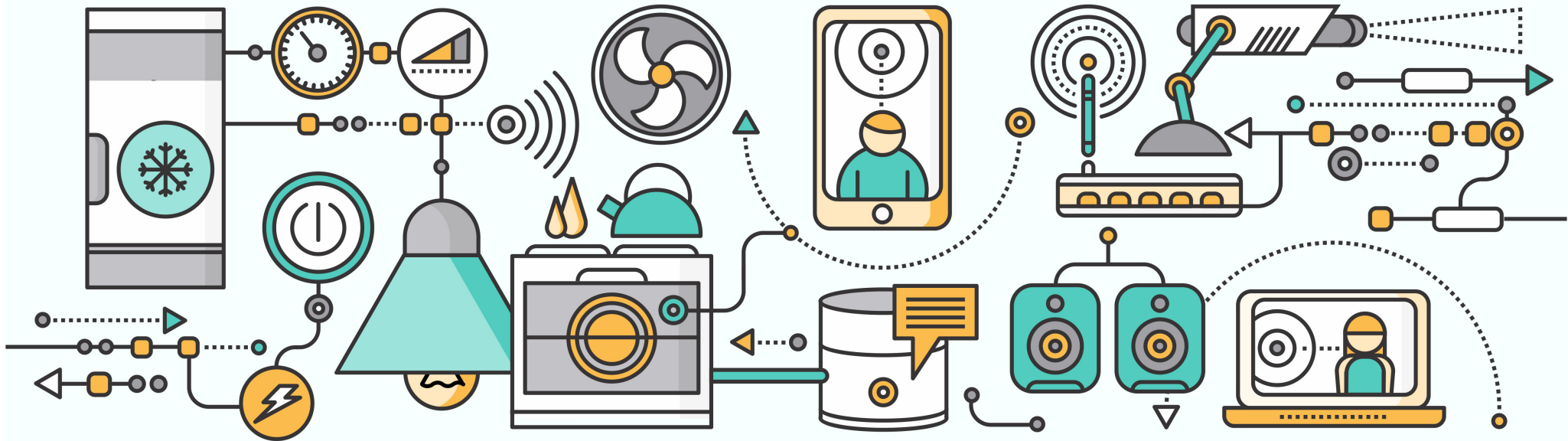


# ENME 441

## Mechatronics and the Internet of Things



## Shift Registers

## **Input shift register:** parallel input, serial output

- Load multiple voltages from different input pins in parallel
- Shift each input voltage to a serial output to be read by the Pi
- Common 8-bit input shift register: TI SN74HC165


## **Output shift register:** serial input, parallel output

- Send multiple voltages in series from the Pi
- Shift each voltage to a different output pin for parallel outputs
- Common 8-bit output shift register: TI SN74HC595


# Latching Output Shift Registers

- **Shift register** = serial-to-parallel converter
  - binary sequence of serial input data → parallel output data block.
  - Allows multiple outputs to be controlled from a single GPIO pin.
- **Latching** = output values are loaded sequentially and applied to all outputs simultaneously on a latch signal
- Shift registers **isolate GPIO pins** from high-current outputs
- Serial, Clock, Latch, and Output pins:
  - **Serial** → serial input data
  - **Clock** → shift register data one step, and place current input in 1<sup>st</sup> register
  - **Latch** → move all register data to parallel output lines simultaneously
  - **Output** → set of parallel output lines


# Output Shift Register Operation

 


# Output Shift Register Operation

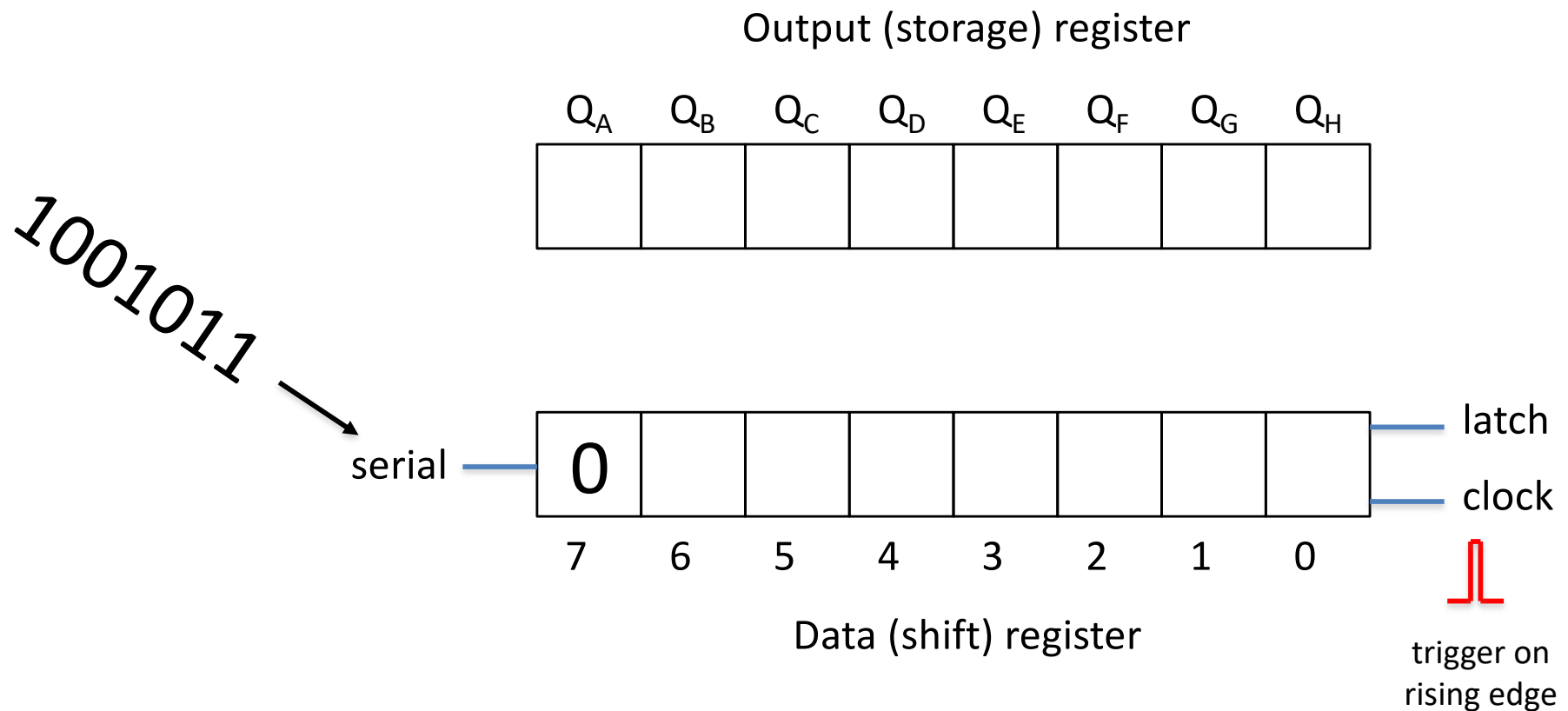


# Output Shift Register Operation

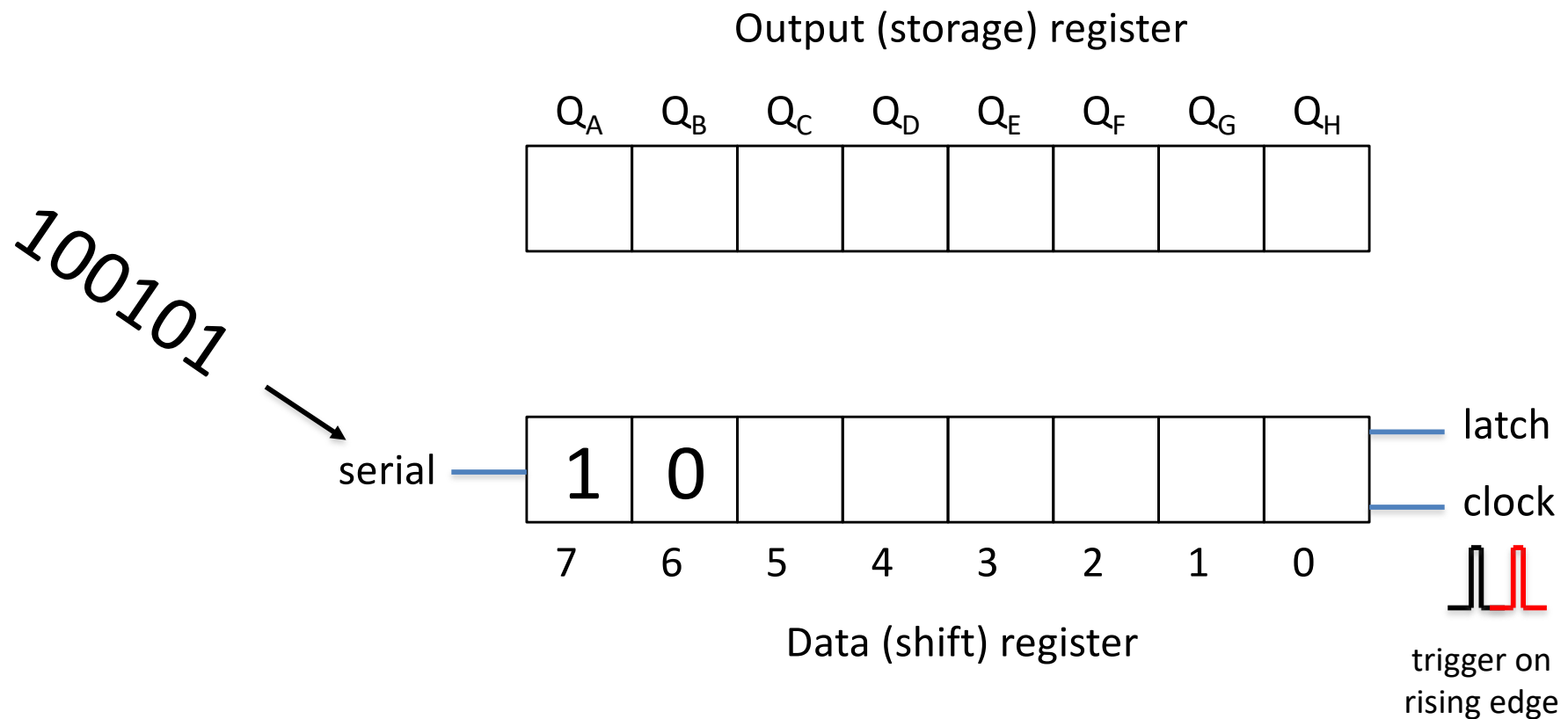

# Output Shift Register Operation

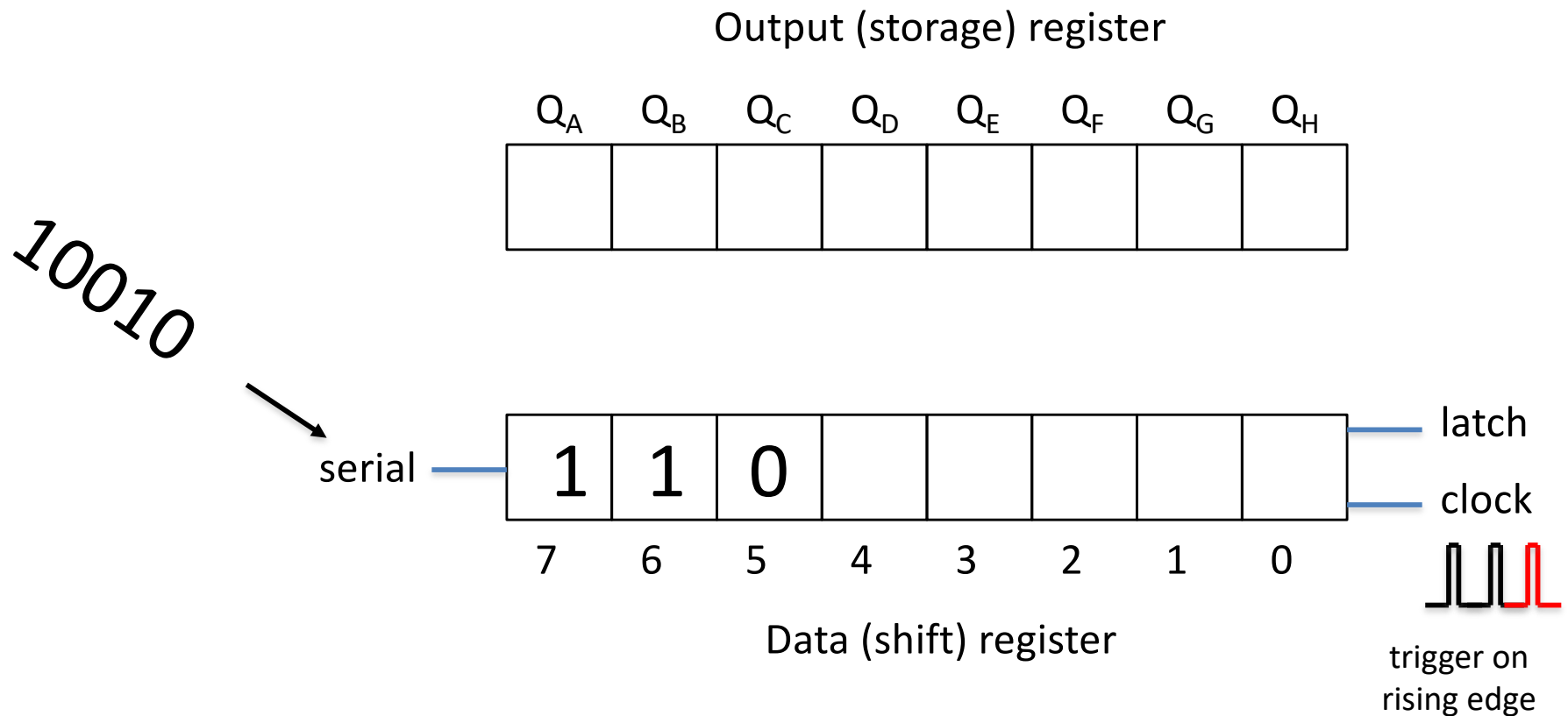


# Output Shift Register Operation

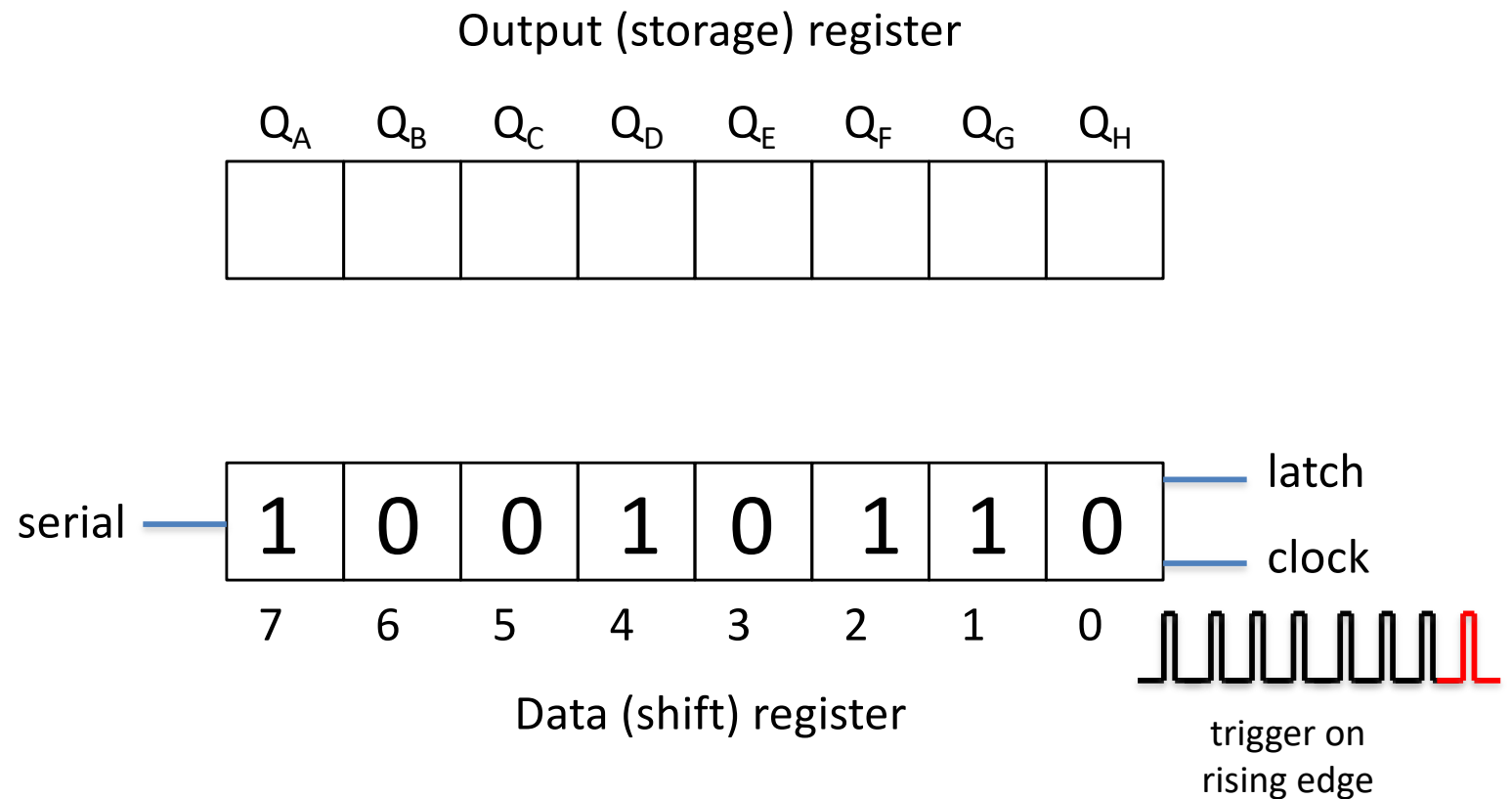





# Output Shift Register Operation

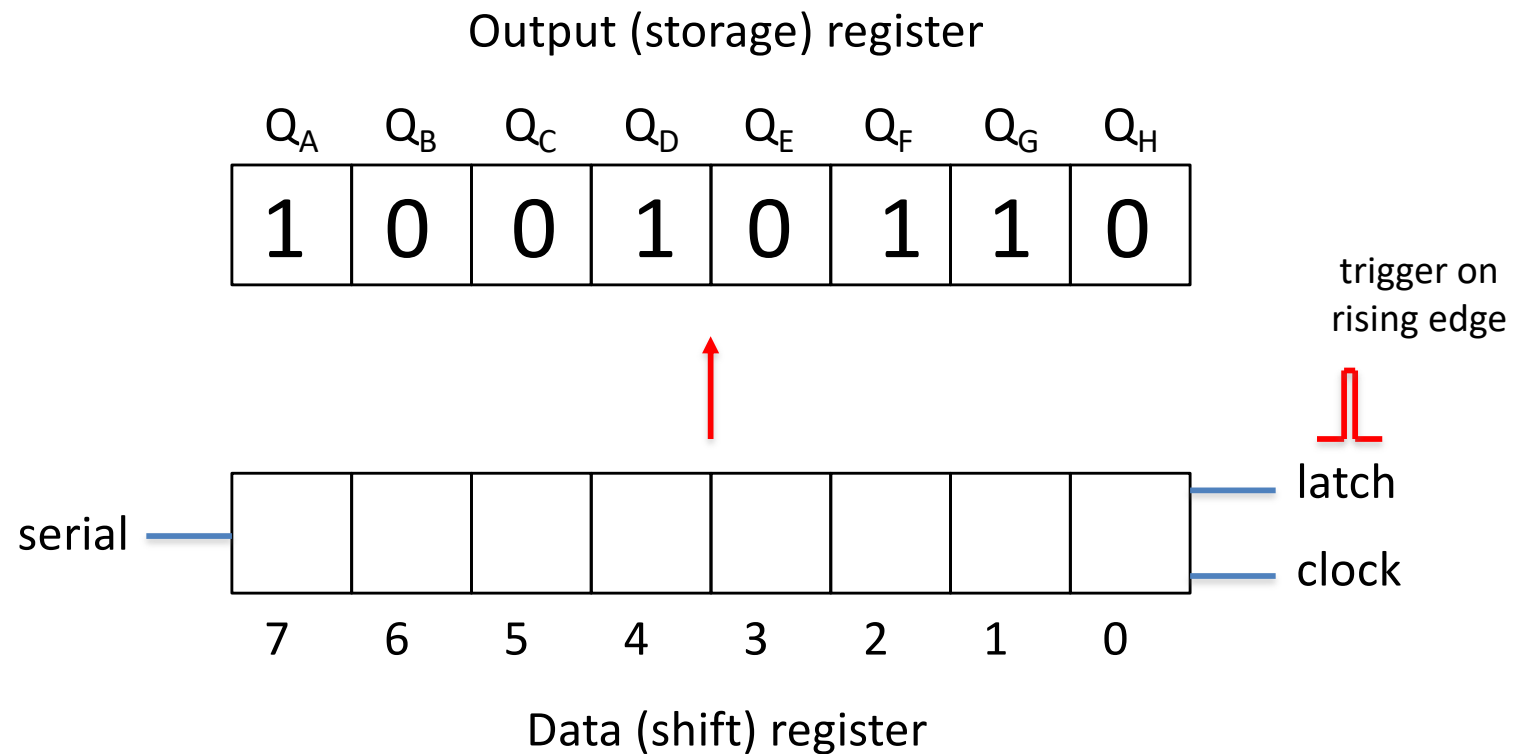


# Cascaded Shift Registers

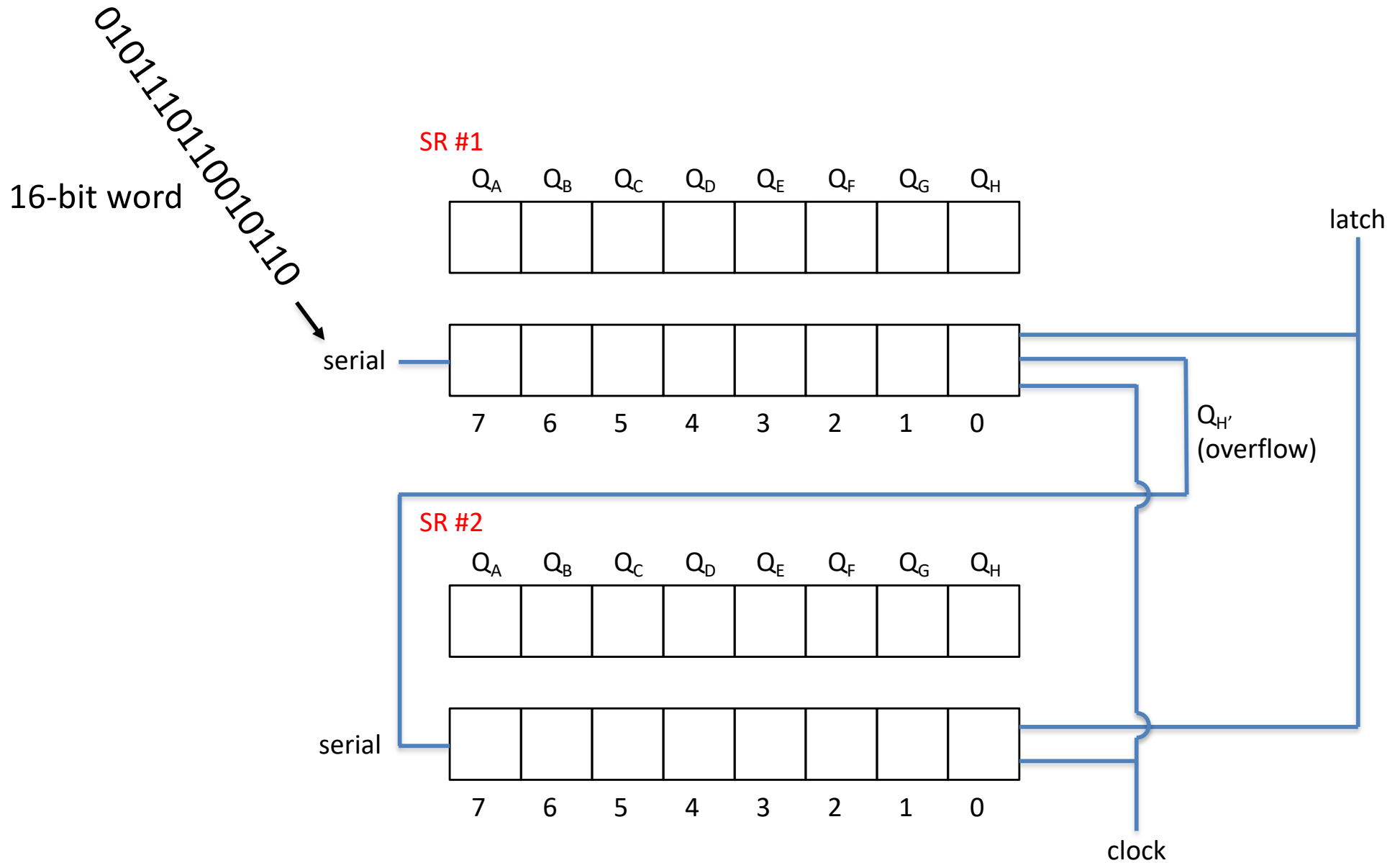


# Cascaded Shift Registers

 


# Cascaded Shift Registers

 

# Cascaded Shift Registers

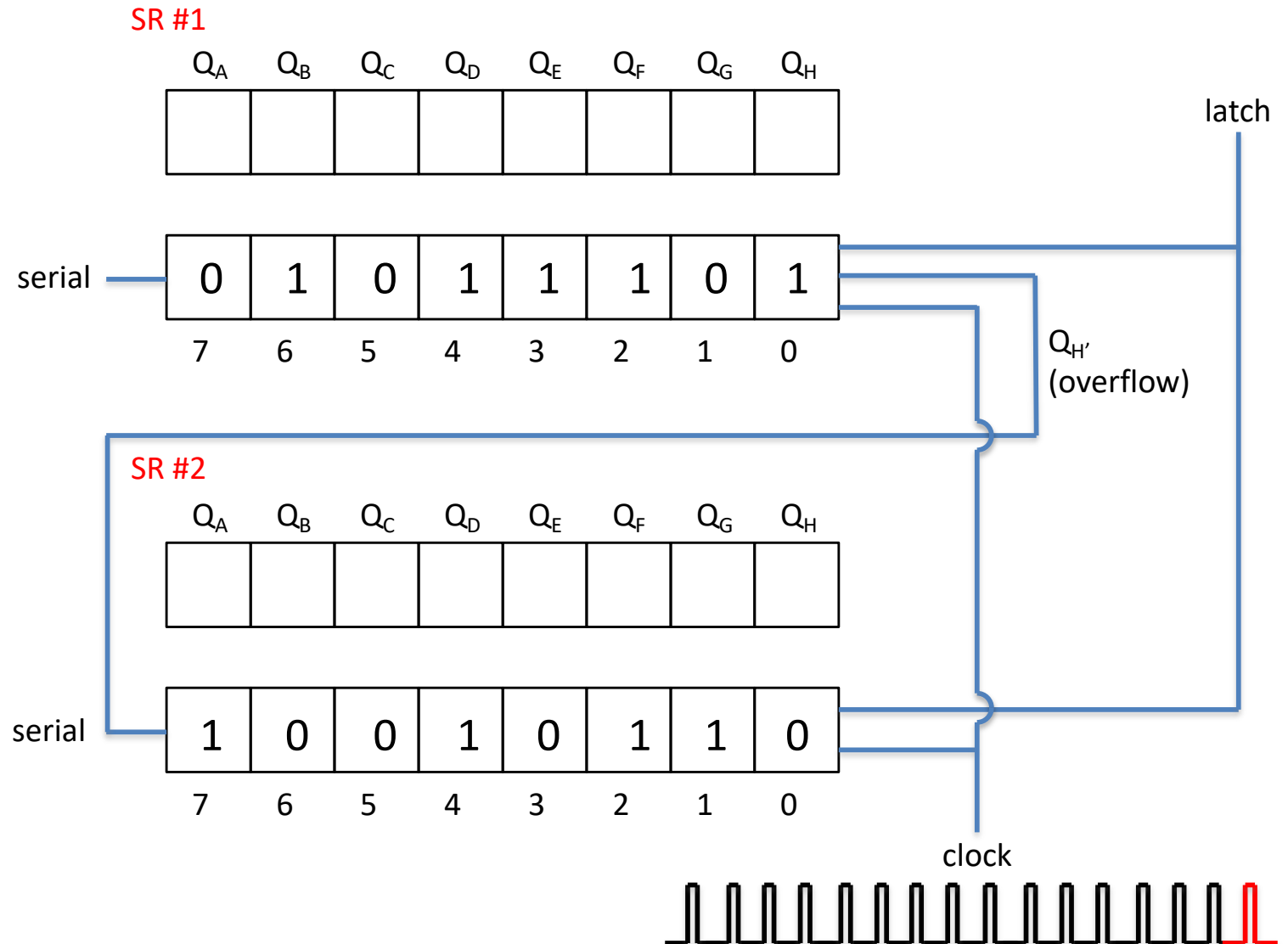


# Cascaded Shift Registers

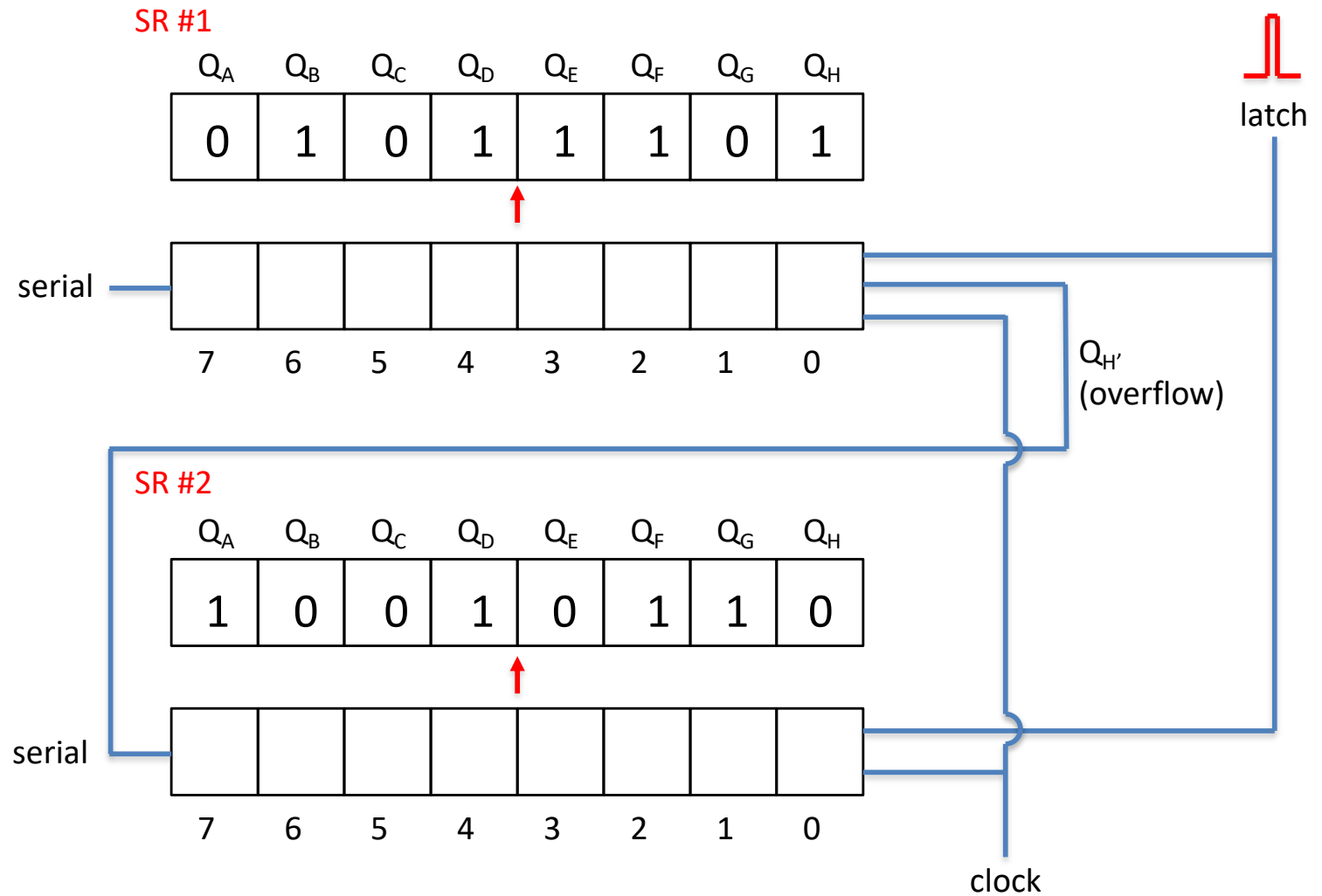

# SN74HC595 Pinout (DIP-16 package)

$\pm 6\text{-mA}$  Output Drive at 5 V


Latching shift register

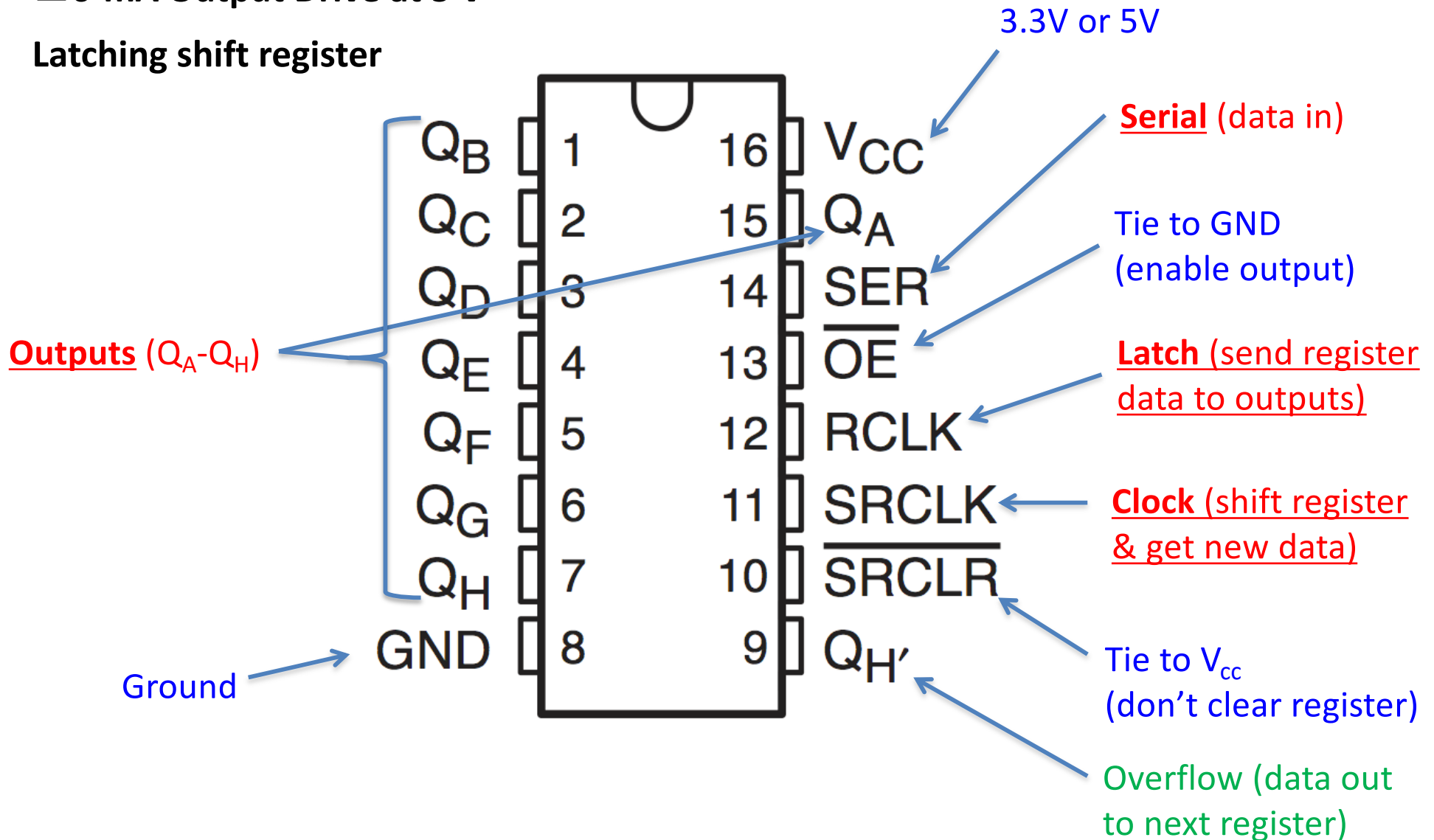
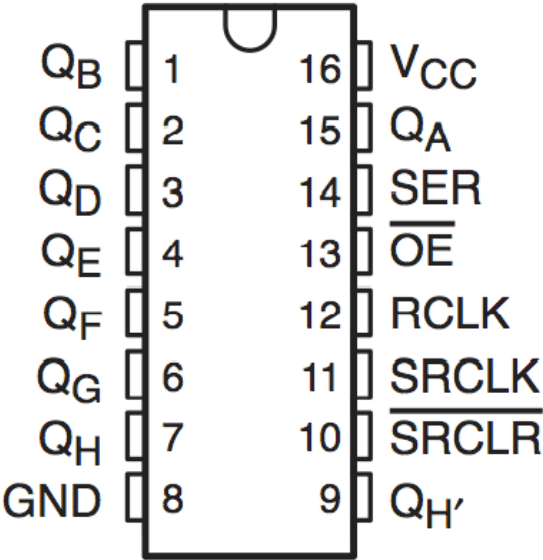
# SN74HC595 Datasheet

OE = output-enable  
SRCLR = shift register clear

SER = serial input (binary data)  
SRCLK = shift register clock ("clock")  
RCLK = storage register clock ("latch")



INPUTS					FUNCTION
SER	SRCLK	SRCLR	RCLK	OE	
X	X	X	X	H	Outputs QA–QH are disabled.
X	X	X	X	L	Outputs QA–QH are enabled.
X	X	L	X	X	Shift register is cleared.
L	↑	H	X	X	First stage of the shift register goes low. Other stages store the data of previous stage, respectively.
H	↑	H	X	X	First stage of the shift register goes high. Other stages store the data of previous stage, respectively.
X	X	X	↑	X	Shift-register data is stored in the storage register.



```

import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110          # pattern to display

for i in range(8):
    GPIO.output(dataPin, pattern & (1<<i))
    GPIO.output(clockPin, 1)    # ping the clock pin to shift register data
    time.sleep(0)
    GPIO.output(clockPin, 0)

GPIO.output(latchPin, 1)       # ping the latch pin to send register to output
time.sleep(0)
GPIO.output(latchPin, 0)

try:
    while 1: pass
except:
    GPIO.cleanup()

```

**Download `shift_reg_initial.py`  
to your Pi by updating from the ENME441  
github repository:**

```

cd ~/enme441-pi
git pull

```

- ***Repeating code...move to a function called ping()***

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110          # pattern to display

for i in range(8):
    GPIO.output(dataPin, pattern & (1<<i))
    GPIO.output(clockPin, 1)    # ping the clock pin to shift register data
    time.sleep(0)
    GPIO.output(clockPin, 0)

GPIO.output(latchPin, 1)       # ping the latch pin to send register to output
time.sleep(0)
GPIO.output(latchPin, 0)

try:
    while 1: pass
except:
    GPIO.cleanup()
```

**Download `shift_reg_initial.py` to your Pi by updating from the ENME441 github repository:**

```
cd ~/enme441-pi
git pull
```

- *Repeating code...move to a function called ping()*

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110 # pattern to display

def ping(p):          # ping the clock or latch pin
    GPIO.output(p,1)
    time.sleep(0)
    GPIO.output(p,0)

for i in range(8):
    GPIO.output(dataPin, pattern & (1<<i))
    ping(clockPin)      # ping the clock pin to shift register data

ping(latchPin)          # ping the latch pin to send register to output

try:
    while 1: pass
except:
    GPIO.cleanup()
```

- ***Move byte shifting to a new function***

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110 # pattern to display

def ping(p):          # ping the clock or latch pin
    GPIO.output(p,1)
    time.sleep(0)
    GPIO.output(p,0)

for i in range(8):
    GPIO.output(dataPin, pattern & (1<<i))
    ping(clockPin)      # ping the clock pin to shift register data

ping(latchPin)          # ping the latch pin to send register to output

try:
    while 1: pass
except:
    GPIO.cleanup()
```

- ***Move byte shifting to a new function***

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110 # pattern to display

def ping(p):          # ping the clock or latch pin
    GPIO.output(p,1)
    time.sleep(0)
    GPIO.output(p,0)

def shiftByte(b):      # send a byte of data to the output
    for i in range(8):
        GPIO.output(dataPin, b & (1<<i))
        ping(clockPin)    # add bit to register
        ping(latchPin)    # send register to output

try:
    shiftByte(0b01100110) # test out the new function
    while 1: pass
except:
    GPIO.cleanup()
```

- ***Display an 8-bit binary counter***

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110 # pattern to display

def ping(p):          # ping the clock or latch pin
    GPIO.output(p,1)
    time.sleep(0)
    GPIO.output(p,0)

def shiftByte(b):      # send a byte of data to the output
    for i in range(8):
        GPIO.output(dataPin, b & (1<<i))
        ping(clockPin)    # add bit to register
        ping(latchPin)    # send register to output

try:
    shiftByte(0b01100110) # test out the new function
    while 1: pass
except:
    GPIO.cleanup()
```

- ***Display an 8-bit binary counter***

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110 # pattern to display

def ping(p):          # ping the clock or latch pin
    GPIO.output(p,1)
    time.sleep(0)
    GPIO.output(p,0)

def shiftByte(b):      # send a byte of data to the output
    for i in range(8):
        GPIO.output(dataPin, b & (1<<i))
        ping(clockPin)    # add bit to register
        ping(latchPin)    # send register to output

try:
    while 1:
        for i in range(2**8):
            shiftByte(i)
            time.sleep(0.5)
except:
    GPIO.cleanup()
```

- ***Move to a new Shifter class***

```
import RPi.GPIO as GPIO
import time

GPIO.setmode(GPIO.BCM)

dataPin, latchPin, clockPin = 23, 24, 25

GPIO.setup(dataPin, GPIO.OUT)
GPIO.setup(latchPin, GPIO.OUT, initial=0) # start latch & clock low
GPIO.setup(clockPin, GPIO.OUT, initial=0)

pattern = 0b01100110 # pattern to display

def ping(p):          # ping the clock or latch pin
    GPIO.output(p,1)
    time.sleep(0)
    GPIO.output(p,0)

def shiftByte(b):      # send a byte of data to the output
    for i in range(8):
        GPIO.output(dataPin, b & (1<<i))
        ping(clockPin)    # add bit to register
        ping(latchPin)    # send register to output

try:
    while 1:
        for i in range(2**8):
            shiftByte(i)
            time.sleep(0.5)
except:
    GPIO.cleanup()
```